# ARTICLE

Considerations for Optimal Capacitive Coupling



#### **INTRODUCTION**

Capacitors used in coupling and DC blocking applications serve to couple RF energy from one part of a circuit to another and are implemented as series elements. Proper selection of coupling capacitors insures the maximum transfer of RF energy. All capacitors will block DC by definition; however, considerations for satisfying the requirements of a coupling application depend on various frequency-dependent parameters that must be taken into account beforehand.



Figure 1. Interstage Coupling Block Diagram

**Figure 1** illustrates two RF amplifier stages operating in a 50-ohm network interconnected by coupling capacitor  $C_0$ . **Table 1** outlines several device options for achieving interstage coupling at various wireless frequencies. Electrical parameters such as the series resonant frequency ( $F_{sR}$ ), parallel resonant frequency ( $F_{PR}$ ), net impedance, insertion loss, equivalent series resistance (ESR) and Q must be evaluated in order to achieve an optimal coupling solution.

**Note:** Coupling capacitor C in **Figure 1** is represented with its equivalent series resistance (ESR) denoted as  $R_{s'}$  equivalent series inductance (ESL) denoted as  $L_{s}$  and parasitic parallel capacitance  $C_{p'}$ , associated with the parallel resonant frequency ( $F_{p_R}$ ).

A capacitor's series resonant frequency ( $\rm F_{\rm sR}$ ) also referred to as self-resonance, occurs at

$$F_{SR} = \frac{1}{2\Pi \sqrt{L_S C_0}}$$

At this frequency the capacitor's net reactance is zero and the impedance is equal to the ESR. As shown in **Table 1**, a KYOCERA AVX 100A101, (100 pF) porcelain capacitor has an F of 1GHz with a corresponding ESR of 0.072 ohms. At this frequency the capacitor will provide its lowest impedance path making it an ideal coupling element. In contrast the impedance of a capacitor at its parallel resonant frequency ( $F_{PR}$ ) can be precipitously high. By assessing the magnitude of S21 vs. frequency for a given capacitor, extreme losses associated with  $F_{PR}$  at the frequency of interest can be readily observed. In coupling applications a capacitor's  $F_{SR}$  can usually be exceeded to some extent without posing a problem as long as the net impedance remains low.

### **NET IMPEDANCE**

The magnitude of a capacitor's impedance is equal to

$$\sqrt{(ESR)^2 + (X_L - X_C)^2}$$

As seen by this relationship a capacitor's impedance is significantly influenced by its net reactance ( $X_c - X_L$ ). It is important to know the magnitude of the impedance throughout the desired passband. A properly selected coupling capacitor will exhibit suitably low impedance at these frequencies.

As seen in Figure 2 the net impedance below  $F_{_{SR}}$  is capacitive and is dominated by  $1/\omega C$  yielding a hyperbolic relationship for frequencies less than  $F_{_{SR}}$ . Conversely, the net impedance above  $F_{_{SR}}$  is inductive and is dominated by  $\omega L$  yielding a linear relationship for frequencies greater than  $F_{_{SR}}$ .

Frequency (MHz)	Device Options	FSR (MHz)	Insertion Loss S21 (dB)	ESR (ohms)	Package Size
900	100A101 – 100 pF	1000	< 0.1	0.072	55 mil x 55 mil
	600S101 – 100 pF	1340	< 0.1	0.070	0603
1900	100A270 – 27 pF	1870	< 0.1	0.161	55 mil x 55 mil
	600S560 – 56 pF	1890	< 0.1	0.085	0603
2400	100A160 – 16 pF	2410	< 0.1	0.218	55 mil x 55 mil
	600S390 – 39 pF	2340	< 0.1	0.140	0603

 Table 1. Examples of Coupling Capacitors and Associated

 Parameters



Figure 2. Impedance vs. Frequency for KYOCERA AVX 100A101 (100pF)

#### **INSERTION LOSS (S21)**

One of the fundamental considerations for all coupling applications is the capacitor's insertion loss at the operating frequency. By evaluating the magnitude of S21 the designer can readily determine whether or not the subject capacitor is suitable. It is especially important to look for the presence of one or more parallel resonances falling within the operating passband. These resonances will generally show up as distinct attenuation notches at their frequencies of occurrence. If a parallel resonance does fall within the operating passband it will be necessary to evaluate its depth in order to determine whether or not the loss is acceptable. In many instances the magnitude of S21 for a given capacitor may be excessive, rendering



it unusable for the application. An insertion loss of several tenths of a dB is generally an acceptable criterion for most coupling applications. Losses that exceed several tenths of a dB within the passband could easily compromise the end performance of a circuit design. Therefore the decision is ultimately left up to the discretion of the designer to determine whether or not these losses are acceptable for a particular design requirement.



**Figure 3.** Insertion Loss vs. Frequency for KYOCERA AVX 100A101, 100pF Chip Capacitor in Flat Mount Orientation

**Figure 3** illustrates the insertion loss characteristic of a KYOCREA AVX 100A101 (100pF) capacitor. The sample was measured in a series through configuration from 50 MHz to 4 GHz with the capacitor's electrodes parallel to the substrate, i.e. flat mount orientation. As seen in **Figure 3** the capacitor's insertion loss is less than 0.1 dB between 200 MHz to 1.5 GHz. By edge mounting the capacitor, i.e. electrodes perpendicular to the substrate, the first parallel resonant notch at 1.6 GHz will be suppressed. As a result the usable frequency range will be extended to approximately 2.4 GHz. In this orientation the same capacitor can be used to extend frequency coverage making it suitable for broadband coupling applications.

#### **ESR AND Q**

ESR is the summation of all series losses in a capacitor and is typically expressed as milli-ohms. ESR losses are comprised of both dielectric loss ( $R_{sD}$ ), and metal loss ( $R_{sM}$ ). **ESR = R\_{sD} + R\_{sM}**.

**Dielectric loss (R\_{sp})** is determined by the specific charSaDcteristics of the dielectric material. Each dielectric material has an associated loss factor most commonly referred to as the loss tangent or dissipation factor (DF). The effect of this loss will cause the dielec-tric to heat. In extreme cases thermal breakdown due to this loss factor may lead to catastrophic device failure. The dissipation factor (DF) provides a good indication of dielectric loss, and is typically characterized at low frequencies i.e. 1MHz, where this loss factor is pre-dominant.

**Metal loss (RSM)** is determined by the specific conductive properties of all metallic materials in the capacitor's construction. This includes electrodes, terminations plus any other metals such as barrier layers etc. The effect of  $R_{_{SM}}$  will also cause heating of the capacitor. In extreme cases thermal breakdown may lead to catastrophic failure. These losses encompass 'skin effect' at higher frequencies and follow a  $\sqrt{f}$  relationship.

Catalog ESR curves typically denote ESR values for frequencies where the losses are predominantly due to the metal. At these frequencies the dielectric losses are negligible and do not significantly influence the overall ESR.

A capacitor's quality factor (Q) is numerically equal to the ratio of its net reactance ( $X_c - X_L$ ) to its equivalent series resistance

$$Q = \frac{X_{N}}{ESR}$$
, where  $X_{N}$  = net reactance =  $|X_{L} - X_{C}|$ 

From this expression it can be seen that the capacitor's Q varies inversely to its ESR and directly with the net reactance. A capacitor's ESR should be known at all frequencies within the passband especially at frequencies above the capacitor's  $F_{sR}$ . At the fre-quency where 'skin effect' has started to effect ohmic losses, the ESR will increase as the  $\sqrt{f}$ , for increasing frequencies. This becomes the dominant loss factor. As previously mentioned an attenuation notch will occur at thecapacitor's  $F_{PR'}$  the depth of which is inversely proportional to the ESR. Therefore the capacitor's ESR will largely determine the depth of the attenuation notch at the parallel resonant frequency.

#### **CONCLUSION**

In conclusion, this article has outlined the importance of frequency dependent characteristics of capacitors in coupling applications. Designing for these applications requires knowledge of a capacitor's series and parallel resonant frequencies, its ESR, as well as its impedance characteristics within the frequency range of interest. Premium suppliers such as KYOCERA AVX provide detailed technical information, which includes S-Parameter files and design software. This affords the designer the flexibility to select various options to meet the most stringent performance requirements.



Table 2. Relationship between ESR, Q, DF and Xc



inquiry@kyocera-avx.com



**NORTH AMERICA** Tel: +1 864-967-2150

**CENTRAL AMERICA** 

Tel: +55 11-46881960

**EUROPE** Tel: +44 1276-697000

**JAPAN** Tel: +81 740-321250

**ASIA** Tel: +65 6286-7555

**NOTICE:** Specifications are subject to change without notice. Contact your nearest KYOCERA AVX Sales Office for the latest specifications. All statements, information and data given herein are believed to be accurate and reliable, but are presented without guarantee, warranty, or responsibility of any kind, expressed or implied. Statements or suggestions concerning possible use of our products are made without representation or warranty that any such use is free of patent infringement and are not recommendations to infringe any patent. The user should not assume that all safety measures are indicated or that other measures may not be required. Specifications are typical and may not apply to all applications.

## in f ୬ ⊙ ► www.kyocera-avx.com